

# Alternating-Current Circuits

Xin Wan (*Zhejiang Univ.*)

Lecture 13

# Outline

- Electromagnetic  $LC$  Oscillations
- Damped Oscillations in an  $RLC$  Circuit
- Forced Oscillations

# LC Oscillations

- In  $RL$  and  $RC$  circuits charge, current, and potential difference **grow and decay exponentially**. The time scale of the growth or decay is given by a time constant  $\tau$ , either capacitive or inductive.

$$\tau_C = RC, \quad \tau_L = L/R$$

- Not surprisingly, we obtain from dimension analysis that

$$\tau_{LC} = \sqrt{LC}$$

is also a time constant, characteristic of an  $LC$  circuit.

- Therefore, one expects in the case of an  $LC$  circuit charge, current, and potential difference **vary periodically (sinusoidally)**. The resulting oscillations of the capacitor's electric field and the inductor's magnetic field are said to be **electromagnetic oscillations**. Such a circuit is said to oscillate.
- In the *ideal*  $LC$  circuit with no resistance, the oscillations continue indefinitely, because of the conservation of energy. There are no energy transfers other than that **between the electric field of the capacitor and the magnetic field of the inductor**.


- We can put in a voltmeter to measure the time-varying potential difference (or voltage)  $v_C$  that exists across the capacitor  $C$ :

$$v_C = q/C,$$

which allows us to find  $q$ .

- Current, as measured by an ammeter, is

$$i = dq/dt.$$

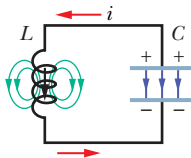

# The Electrical–Mechanical Analogy

Block–Spring System		$LC$ Oscillator	
Element	Energy	Element	Energy
Spring	Potential, $\frac{1}{2}kx^2$	Capacitor	Electrical, $\frac{1}{2}(1/C)q^2$
Block	Kinetic, $\frac{1}{2}mv^2$	Inductor	Magnetic, $\frac{1}{2}Li^2$
$v = dx/dt$		$i = dq/dt$	

- These correspondences then suggest that
  - $q$  corresponds to  $x$ ,  $1/C$  corresponds to  $k$ ,
  - $i$  corresponds to  $v = dx/dt$ , and  $L$  corresponds to  $m$ .
- The angular frequency of the oscillation for an ideal (resistanceless)  $LC$  circuit is then (analogous to  $\sqrt{k/m}$ )

$$\omega_0 = 1/\tau_{LC} = 1/\sqrt{LC}.$$

# LC Oscillations – A Quantitative Analysis

- The total energy  $U$  in an oscillating  $LC$  circuit is given by

$$U = U_B + U_E = \frac{Li^2}{2} + \frac{q^2}{2C}.$$

- In the absence of resistance,  $U$  remains constant with time.

$$\frac{dU}{dt} = \frac{d}{dt} \left( \frac{Li^2}{2} + \frac{q^2}{2C} \right) = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = 0.$$

With  $i = dq/dt$  and  $di/dt = d^2q/dt^2$ , we find

$$L \frac{d^2q}{dt^2} + \frac{1}{C} q = 0.$$

- We have obtained the differential equation that describes the oscillations of a resistanceless  $LC$  circuit.
- This contrasts with the mechanical form

$$m \frac{d^2 x}{dt^2} + kx = 0,$$

whose general solution is

$$x = A \cos(\omega_0 t + \phi),$$

where  $\omega_0 = \sqrt{k/m}$  is an intrinsic property of the block-spring system.



- By analogy, we can write the general solution for the  $LC$  circuit as

$$q = Q \cos(\omega_0 t + \phi),$$

where  $\omega_0 = 1/\sqrt{LC}$  is an intrinsic property of the circuit.

- $Q$  is the amplitude of the charge variations, and  $\phi$  is the phase constant. These two constants can be determined by, e.g., initial conditions,

$$Q \cos \phi = q|_{t=0},$$

$$-\omega_0 Q \sin \phi = \left. \frac{dq}{dt} \right|_{t=0} \equiv i|_{t=0}.$$

- Note that the second initial condition can be understood by taking the first derivative of charge  $q$  with respect to time  $t$ , which gives us the current:


$$i = -I \sin(\omega_0 t + \phi) = I \cos(\omega_0 t + \phi'),$$


where  $I = \omega_0 Q$  and  $\phi' = \phi + \pi/2$ .

- In other words, current leads charge (or voltage across the capacitor) in phase by  $\pi/2$ .


- Therefore, electrical energy and magnetic energy oscillate.
  - The maximum values of  $U_E$  and  $U_B$  are both  $Q^2/2C$ .
  - At any instant the sum of  $U_E$  and  $U_B$  is equal to  $Q^2/2C$ , a constant.
  - When  $U_E$  is maximum,  $U_B$  is zero, and conversely.

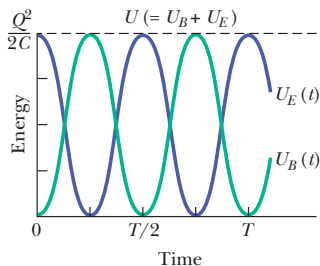The electrical and magnetic energies vary but the total is constant.




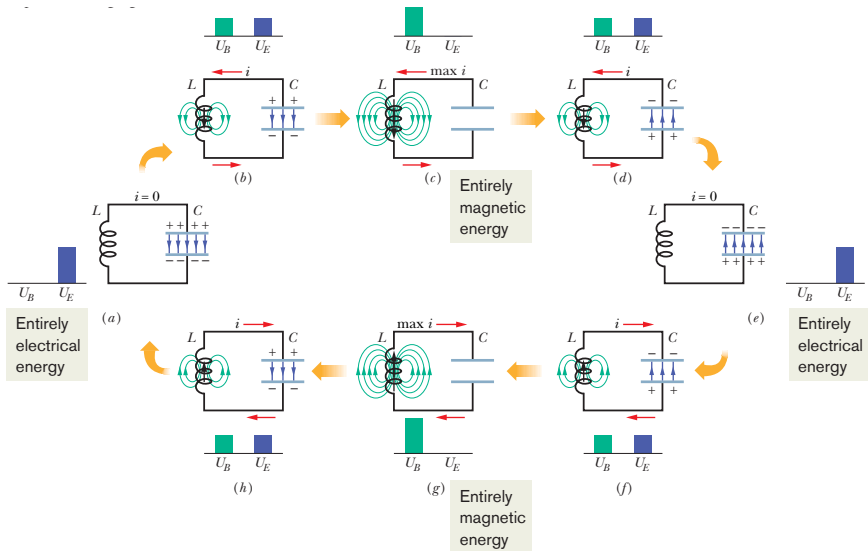

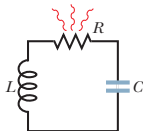- In an *actual*  $LC$  circuit, the oscillations will not continue indefinitely because there is always some resistance present that will drain energy from the electric and magnetic fields and dissipate it as *thermal energy* (the circuit may become warmer).



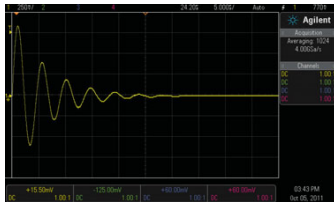- This is similar to the decay of mechanical oscillations caused by frictional damping in a block-spring system.



# The Complex Formalism

- In an  $RC$  circuit, the general solution is, up to a constant,

$$q = Qe^{-t/\tau}.$$

- In an  $LC$  circuit, the general solution is,

$$q = Q \cos(\omega_0 t + \phi) = \Re [Qe^{i\omega_0 t} e^{i\phi}].$$

- We can write down the more general solution as

$$q = \Re [\tilde{Q}e^{i\tilde{\omega}t}] = Qe^{-t/\tau} \cos(\omega t + \phi),$$

where we define a complex amplitude  $\tilde{Q} = Qe^{i\phi}$  and a complex frequency  $\tilde{\omega} = \omega + i/\tau$ .

# Damped Oscillations in an $RLC$ Circuit

- With a resistance  $R$  present, the total electromagnetic energy  $U$  of the circuit is no longer constant; instead, it decreases with time as energy is transferred to thermal energy in the resistance:

$$\frac{dU}{dt} = -i^2 R.$$

- Because of this loss of energy, the oscillations of charge, current, and potential difference continuously decrease in amplitude, and the oscillations are said to be **damped**, just as with the damped block-spring oscillator.

- The differential equation for damped oscillations in an  $RLC$  circuit is then

$$\frac{dU}{dt} = Li \frac{di}{dt} + \frac{q}{C} \frac{dq}{dt} = -i^2 R.$$

With  $i = dq/dt$  and  $di/dt = d^2q/dt^2$ , we find


$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0.$$

- Plugging in  $q = \tilde{Q}e^{i\tilde{\omega}t}$ , we obtain

$$-L\tilde{\omega}^2 + i\tilde{\omega}R + \frac{1}{C} = 0.$$



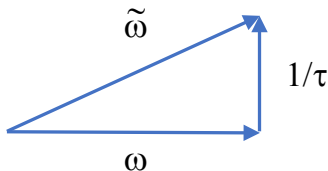- By introducing the complex formalism, we transform the second-order differential equation to a quadratic equation in the complex frequency, which can then be solved by the quadratic formula.




- We can further assume that  $\omega$  is positive, because we are only interested in the real part of the solution

$$q = Qe^{-t/\tau} \cos(\omega t + \phi).$$

- The solution for  $\tilde{\omega} = \omega + i/\tau$  satisfies

$$\omega = \sqrt{\omega_0^2 - (1/\tau)^2} \quad \text{and} \quad 1/\tau = R/(2L),$$

in which  $\omega_0 = |\tilde{\omega}| = 1/\sqrt{LC}$ .

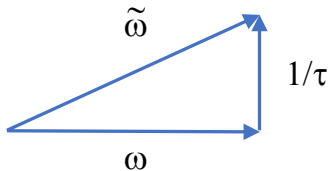

- What happens when the damping is very strong?


- When  $1/\tau < \omega_0$ , a real  $\omega$  can be found and the system still oscillates, but with decreasing amplitude as its energy is converted to heat. The circuit is said to be **underdamped**. Over time the system should come to rest at equilibrium.
- When  $1/\tau > \omega_0$ , one can only find imaginary  $\omega$ , which means the frictional force is so great that the system cannot oscillate. The circuit is said to be **overdamped**.
- In between, when  $1/\tau = \omega_0$ , the circuit is said to be **critically damped**. It is worth noting that *the critical damping gives the fastest return of the system to its equilibrium position*. In engineering design this is often a desirable property.

# AC Circuits and Forced Oscillations

- The oscillations in an  $RLC$  circuit will not damp out if an external emf device supplies enough energy to make up for the energy dissipated as thermal energy in the resistance  $R$ .
- The energy is supplied via oscillating emfs and currents — the current is said to be an **alternating current**, or **ac** for short. These oscillating emfs and currents vary sinusoidally with time, reversing direction 100 times per second and thus having frequency  $f = 50$  Hz.

- An ac generator can induce a sinusoidally oscillating emf  $\mathcal{E}$
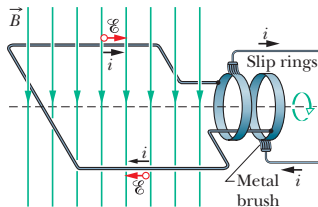
$$\mathcal{E} = \mathcal{E}_m \cos \omega_d t.$$



- When the rotating loop is part of a closed conducting path, this emf drives a sinusoidal current along the path with the same angular frequency  $\omega_d$ , which then is called the **driving angular frequency**. We can write the current as

$$i = I \cos(\omega_d t + \phi).$$

# Natural vs Driving Frequency

- In both undamped  $LC$  circuits and underdamped  $RLC$  circuits (with sufficiently small enough  $R$ ), the charge, potential difference, and current oscillate at the circuit's **natural angular frequency**  $\omega_0 = 1/\sqrt{LC}$ . Such oscillations are said to be **free oscillations**.
- When the external alternating emf is connected, the oscillations of charge, potential difference, and current are said to be **driven oscillations** or **forced oscillations**. These oscillations always occur at the **driving angular frequency**.

# Three Simple Circuits

- Assume the potential difference across a circuit element (resistor, capacitor, and inductor) is

$$v(t) = \Re(\tilde{V}e^{i\omega_d t}),$$

and the current in the element is


$$i(t) = \Re(\tilde{I}e^{i\omega_d t}).$$

- We can define **complex impedance** as

$$\tilde{Z} = Ze^{i\phi} = \frac{\tilde{V}}{\tilde{I}}.$$


- In a resistive load,

$$\tilde{Z} = R.$$

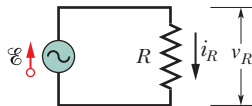

- In an inductive load,


$$\tilde{Z} = i\omega_d L.$$

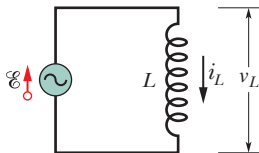

- Notice  $di(t)/dt = (i\omega_d)i(t)$ .

- Similarly, in a capacitive load,

$$\tilde{Z} = \frac{1}{i\omega_d C}.$$

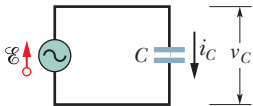




# The Series $RLC$ Circuit

- Combining impedances has similarities to the combining of resistors, but the phase relationships make it practically necessary to use the complex impedance method for carrying out the operations.
- Combining series impedances is straightforward:

$$\tilde{Z} = \tilde{Z}_1 + \tilde{Z}_2.$$

- When  $R$ ,  $L$ , and  $C$  are in series,

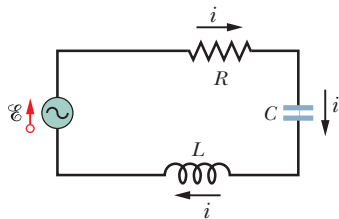
$$\tilde{Z} = R + i \left( \omega_d L - \frac{1}{\omega_d C} \right).$$



- Alternatively, if we write  $\tilde{Z} = Ze^{i\phi}$ , we find

$$Z \cos \phi = R,$$
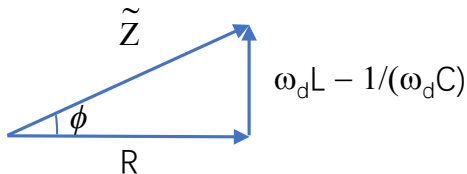
$$Z \sin \phi = \omega_d L - \frac{1}{\omega_d C}.$$




- Therefore, the impedance  $Z$  and the phase constant  $\tan \phi$  are

$$Z = \sqrt{R^2 + [\omega_d L - 1/(\omega_d C)]^2},$$

$$\tan \phi = \frac{\omega_d L - 1/(\omega_d C)}{R}.$$

# Resonance

- When  $\omega_d$  equals  $\omega_0$ , the circuit is in **resonance**.
  - The circuit is equally capacitive and inductive ( $|Z_C| = |Z_L|$ ).
  - The current amplitude  $I = \mathcal{E}_m/R$  is maximum.
  - Current and emf are in phase ( $\phi = 0$ ).
- The low angular-frequency side of a resonance curve is dominated by the capacitor's impedance, and the high angular-frequency side is dominated by the inductor's impedance.

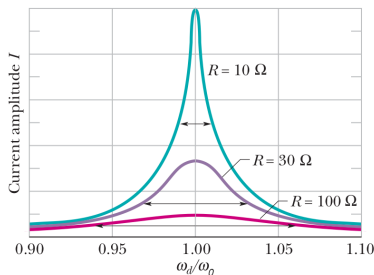

# Summary

- Energy transfers  $U = U_E + U_B$ , where

$$U_E = \frac{q^2}{2C} \qquad U_B = \frac{Li^2}{2}$$

$$\frac{dU}{dt} = -i^2 R$$

- $LC$  oscillations

$$L \frac{d^2 q}{dt^2} + \frac{1}{C} q = 0$$

$$q = Q \cos(\omega_0 t + \phi)$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

- Damped oscillations in an  $RLC$  circuit

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = 0$$

$$q = Q e^{-t/\tau} \cos(\omega t + \phi)$$

$$\omega = \sqrt{\omega_0^2 - (1/\tau)^2}$$

$$1/\tau = R/(2L)$$

- Forced oscillations in a series  $RLC$  circuit at a driving angular frequency  $\omega_d$

$$\mathcal{E} = \mathcal{E}_m \cos \omega_d t$$

$$i = I \cos(\omega_d t + \phi)$$

- Resonance

- The circuit is equally capacitive and inductive:  $1/(\omega_d C) = \omega_d L$ , or  $\omega_d = \omega_0$ .
- $I = I_{\max} = \mathcal{E}_m / R$
- $\phi = 0$

Halliday, Resnick & Krane:

- Chapter 37: Alternating Current Circuits